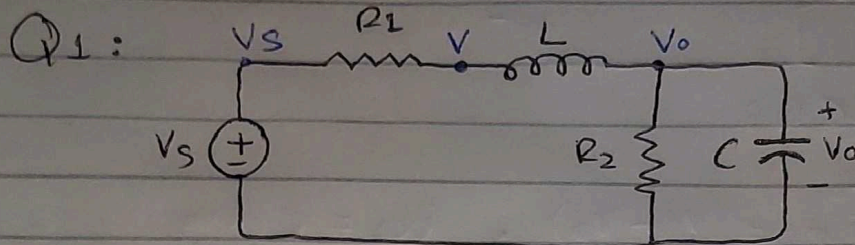


Electric Network Analysis

'Assignment 1'



→ Applying KCL;

$$i_L = i_C + i_{R_2}$$

→ Applying $V_L = V - V_o$;

$$\boxed{\frac{1}{L} \int V_1 - V_o = C \frac{dV_o}{dt} + \frac{V_o}{R_2}}$$

$$\int (V_1 - V_o) = LC \frac{dV_o}{dt} + \frac{L}{R_2} V_o$$

$$\boxed{V_1 = LC \left(\frac{d^2 V_o}{dt^2} \right) + \left(\frac{L}{R_2} \right) \left(\frac{dV_o}{dt} \right) + V_o}$$

→ Applying KVL; (At node V)

$$i_{R_1} = i_L$$

→ Applying $\frac{(V_s - V_1)}{R_1} = i_{R_1}$, $i_L = \frac{1}{L} \int V_1 - V_o$;


$$\boxed{\frac{V_s - V_1}{R_1} = \frac{1}{L} \int V_1 - V_o}$$

→ substitute eq I and II in above eq;

$$\frac{V_s}{R_1} - \frac{1}{R_1} \left(LC \left(\frac{d^2 V_o}{dt^2} \right) + \frac{L}{R_2} \left(\frac{dV_o}{dt} \right) + V_o \right) = C \frac{dV_o}{dt} + \frac{V_o}{R_2}$$

$$\frac{L}{R_2} \left(\frac{dV_o}{dt} \right) + LC \left(\frac{d^2 V_o}{dt^2} \right) + V_o = V_s - CR_1 \left(\frac{dV_o}{dt} \right) + R_1 \left(\frac{V_o}{R_2} \right)$$
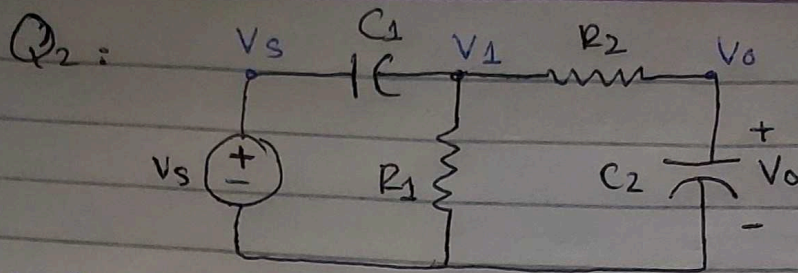
$$\boxed{\frac{d^2 V_o}{dt^2} + \frac{dV_o}{dt} \left(\frac{1}{R_2 C} + \frac{R_1}{L} \right) + V_o \left(\frac{R_1}{R_2 LC} + \frac{1}{LC} \right) = \frac{V_s}{LC}}$$



→ Applying KCL;

$$i_{R2} = i_{C2}$$

→ Applying $i_{R2} = \frac{V_1 - V_0}{R_2}$, $i_{C2} = C_2 \frac{dV_0}{dt}$

$$\frac{V_1 - V_0}{R_2} = C_2 \frac{dV_0}{dt}$$

$$V_1 = R_2 C_2 \frac{dV_0}{dt} + V_0 \quad \text{--- I}$$

→ Substituting above equation in i_{R1} ;

$$i_{R1} = \frac{V_1}{R_1}$$

$$i_{R1} = \frac{R_2 C_2 \left(\frac{dV_0}{dt} \right) + \frac{V_0}{R_1}}{R_1} \quad \text{--- II}$$

→ substituting eq I now in i_{C1} ;

$$i_{C1} = C_1 \frac{d(V_C)}{dt} \quad \text{where } V_C = (V_S - V_1)$$

$$i_{C1} = C_1 \frac{d(V_S - V_1)}{dt}$$

$$i_{C2} = C_1 \left(\frac{dV_S}{dt} - R_2 C_2 \left(\frac{d^2 V_0}{dt^2} \right) - \frac{dV_0}{dt} \right) \quad \text{--- III}$$

→ substitute eq II and III in following equation;

→ Apply KCL;

$$i_{C1} = i_{R1} + i_{C2}$$

$$C_1 \left(\frac{dV_S}{dt} - R_2 C_2 \left(\frac{d^2 V_0}{dt^2} \right) - \frac{dV_0}{dt} \right) =$$

$$\frac{R_2 C_2}{R_1} \left(\frac{dV_0}{dt} \right) + \frac{V_0}{R_1} + C_2 \frac{dV_0}{dt}$$

$$\frac{dV_s}{dt} - R_2 C_2 \left(\frac{d^2 V_o}{dt^2} \right) - \frac{dV_o}{dt} = \frac{R_2 C_2}{R_1 C_1} \left(\frac{dV_o}{dt} \right) + \frac{V_o}{R_1 C_1} + \frac{C_2}{C_1} \frac{dV_o}{dt}$$


→ divide both sides $R_2 C_2$;

$$\frac{dV_s}{R_2 C_2 dt} - \frac{d^2 V_o}{dt^2} - \left(\frac{dV_o}{dt} \right) \frac{1}{R_2 C_2} =$$

$$\left(\frac{dV_o}{dt} \right) \left(\frac{1}{R_1 C_2} \right) + \frac{1}{R_1 R_2 C_1 C_2} (V_o) + \frac{1}{C_1 R_2} \left(\frac{dV_o}{dt} \right)$$


$$\boxed{\frac{d^2 V_o}{dt^2} + \frac{dV_o}{dt} \left(\frac{R_1 C_1 + R_2 C_2 + R_1 C_2}{R_1 R_2 C_1 C_2} \right) + \left(\frac{1}{R_1 R_2 C_1 C_2} \right) V_o = \frac{1}{R_2 C_2} \left(\frac{dV_s}{dt} \right)}$$

ON NEXT PAGE →

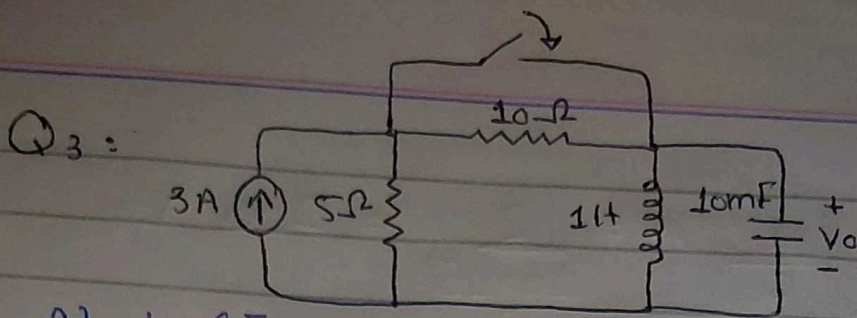

At $t = 0^-$;

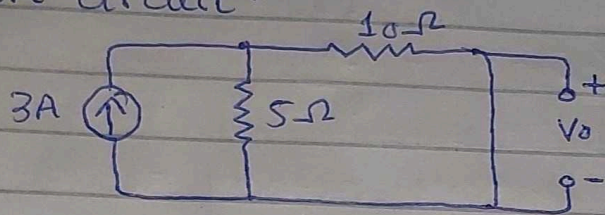→ During the steady state, before the switch activation capacitor acts as an open circuit and inductor as a short circuit.



→ Apply CDR;

$$i_L(0^-) = \frac{5}{10+5} \times 3$$

$$i_L(0^-) = 1 \text{ A}$$


$$\rightarrow V_o(0^-) = 0$$

→ By Continuity rules of capacitance and inductance;

$$i_L(0^-) = I_L(0^+) = 1 \text{ A}$$

$$V_o(0^-) = V_o(0^+) = 0$$

At $t = 0^+$;

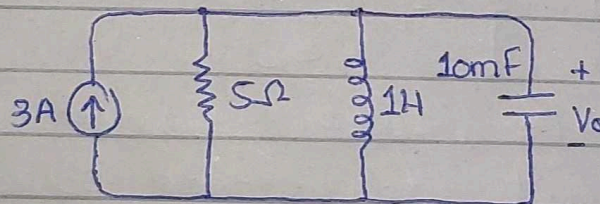

→ By capacitance law;

$$i_c(0^+) = C \frac{dV(0^+)}{dt} \Rightarrow \frac{dV(0^+)}{dt} = \frac{i_c(0^+)}{C}$$

→ Apply KCL;

$$I_s = I_R(0^+) + I_L(0^+) + i_c(0^+)$$

$$3 = \frac{V_o(0^+)}{R} + 1 + i_c(0^+)$$

$$i_c(0^+) = 3 - 1 + 0$$


$$i_c(0^+) = 2 \text{ A}$$

→ Therefore;

$$\frac{d(V(0^+))}{dt} = \frac{i_c(0^+)}{C} = \frac{2}{10 \times 10^{-3}} = 200 \text{ V/s}$$


$$\boxed{\frac{dV(0^+)}{dt} = 200 \text{ V/s}}$$

At $t = \infty$;

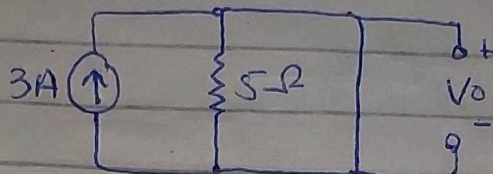

→ At $t = \infty$, circuit reaches steady state again.

$$\boxed{V_o(\infty) = 0}$$

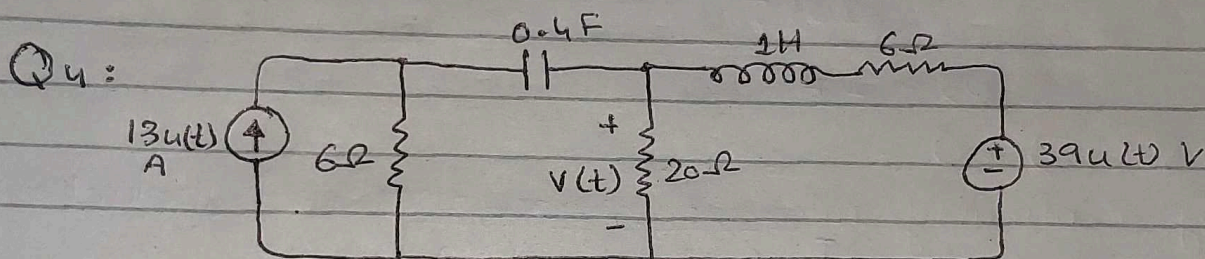


At $t = 0^-$;

→ $u(t)$ is the unit step function defined as;

$$u(t) = \begin{cases} 1 & t \geq 0 \\ 0 & t < 0 \end{cases}$$

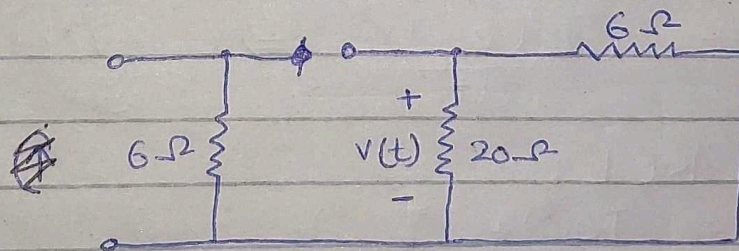So, at $t = 0^-$, current source becomes / acts as open circuit and voltage source acts as short circuit.



→ A circuit is not active;

$$V_c(0^-) = 0$$


$$i_L(0^-) = 0$$

→ By continuity rules of capacitor and inductor;

$$V_C(0^-) = V_C(0^+) = 0$$

$$i_L(0^-) = i_L(0^+) = 0$$

At $t = 0^+$;

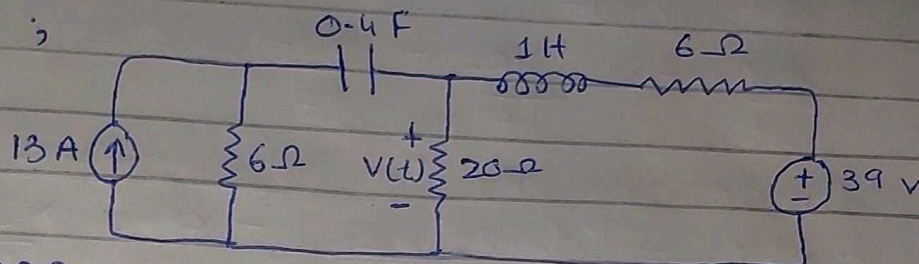

→ By CDR;

$$i(0^+) = \frac{6}{20+6} \times 13$$

$$i(0^+) = 3 \text{ A}$$

→ By Ohm's law;

$$V(0^+) = R \times i(0^+) \\ = 20 \times 3$$

$$V(0^+) = 60 \text{ V}$$

$$\rightarrow V(t) = 20 i_c$$

→ Taking differentiation on both sides;

$$\frac{dV(t)}{dt} = 20 \frac{di_c}{dt}$$

$$\rightarrow \text{Letting } i_c = C \frac{dV_C(0^+)}{dt}$$

$$\rightarrow \text{For } \frac{dV_C(0^+)}{dt};$$

• Apply KCL;

$$i_s = i_{R1} + i$$

$$13 = \frac{V_{R1}}{R_1} + \frac{V}{R_2}$$

$$\frac{V_{R1}}{R_1} = 13 - \frac{V}{R_2} \quad (1)$$

- Apply KVL;

$$V_{R1} = V_C + V$$

$$\frac{dV_{R1}}{dt} = \frac{dV_C}{dt} + \frac{dV}{dt}$$

$$\frac{dV}{dt} = \frac{dV_{R1}}{dt} - \frac{dV_C}{dt}$$

- Divide by R_1 on both sides

$$\frac{1}{R_1} \times \frac{dV}{dt} = \frac{dV_{R1}}{dt} \times \frac{1}{R_1} - \frac{dV_C}{dt} \times \frac{1}{R_1}$$

- Apply capacitance law, $\frac{dV_C}{dt} = \frac{i_C}{C}$;

and put eq 1 in above eq.

$$\frac{dV}{dt} \times \frac{1}{R_1} = \frac{d}{dt} \left(13 - \frac{dV}{dt} \times \frac{1}{R_2} \right) - \frac{i_C}{CR_1}$$

$$\frac{dV}{dt} \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = -\frac{i_C}{CR_1}$$

$$\frac{dV}{dt} = \frac{-i_C}{C} \times \frac{R_2}{(R_1 + R_2)}$$


$$\frac{dV(0^+)}{dt} = \frac{-i_C R_2}{C(R_1 + R_2)}$$

→ substitute respective values;

$$\frac{dV(0^+)}{dt} = -\frac{3 \times 20}{(20 + 6)(0.4)}$$

$$\frac{dV(0^+)}{dt} = 5.77 \text{ V/s}$$

At $t = \infty$;

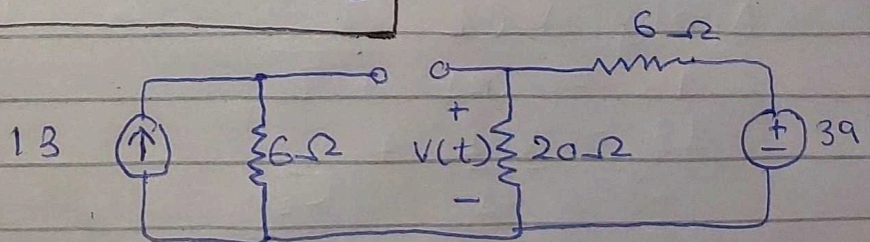

→ By VDR;

$$V(\infty) = \frac{20}{26} \times 39$$

$$V(\infty) = 30 \text{ V}$$

Q5: $\frac{d^2 i}{dt^2} + 2 \frac{di}{dt} + 5i = 10$

→ Source free or natural response of circuit is that response with $V_s = 0$ and $i_s = 0$

$$\frac{d^2 i}{dt^2} + 2 \frac{di}{dt} + 5i = 0 \quad \text{--- (1)}$$

→ $\frac{d^2 y(t)}{dt^2} + 2\zeta\omega_0 \frac{dy(t)}{dt} + \omega_0^2 y(t) = 0 \quad \text{--- (2)}$

→ Comparing eq (1) with eq (2);

$$2\zeta\omega_0 = 2$$

and

$$\omega_0^2 = 5$$

$$\boxed{\zeta = \frac{1}{\sqrt{5}}}$$

$$\boxed{\omega_0 = \sqrt{5}}$$

→ A suggested exponential solution for eq (1);

$$\bullet i(t) = Ae^{st}$$

$$\bullet \frac{di(t)}{dt} = Ase^{st}$$

$$\bullet \frac{d^2 i(t)}{dt^2} = As^2 e^{st}$$

Thus,

$$As^2 e^{st} + 2Ase^{st} + 5Ae^{st} = 0$$

$$\boxed{Ae^{st} (s^2 + 2s + 5) = 0}$$

→ As $\zeta = 1/\sqrt{5}$, $0 < \zeta < 1$, so an underdamped response;

$$\boxed{s_{1,2} = -\zeta\omega_0 \pm (\sqrt{1-\zeta^2})\omega_0}$$

OR

$$\boxed{s_{1,2} = -a \pm j\omega_d}$$

where,

$$a = \zeta\omega_0$$

$$= (1/\sqrt{5})(\sqrt{5})$$

$$\boxed{a = 1 \text{ Np/s}}$$

$$\omega_d = \omega_0 \sqrt{1-\zeta^2}$$

$$= \sqrt{5} \sqrt{1-(1/\sqrt{5})^2}$$

$$\boxed{\omega_d = 2 \text{ rad/s}}$$

→ $i(t)$ and its derivative at $t=0^+$;

- $i(0^+) = 2A$

- $\frac{di(0^+)}{dt} = 4 \text{ A/s}$

→ Let us now find, A and θ on the basis of initial condition,

$$i(t) = A e^{-at} \cos(\omega t + \theta)$$

- $i(0^+) = A e^0 \cos(0 + \theta)$

$$2 = A \cos \theta$$

$$\boxed{A \cos \theta = 2} \quad \text{--- (1)}$$

- $i(t) = A e^{-at} (\cos(\omega t + \theta))$

$$\frac{di(t)}{dt} = A (e^{-at} (-a) (\cos(\omega t + \theta)) + \sin(\omega t + \theta) \omega e^{-at})$$

→ put $a=1$ and $\omega=2$

$$\frac{di(t)}{dt} = A [(e^{-t} - \cos(2t + \theta)) + 2 \sin(2t + \theta) e^{-t}]$$

$$\frac{di(0^+)}{dt} = A [e^0 - \cos \theta + 2 \sin \theta e^0]$$

$$4 = A (2 \sin \theta - \cos \theta)$$

$$\boxed{2A \sin \theta - A \cos \theta = 4} \quad \text{--- (2)}$$

→ Substitute eq (1) and eq (2);

$$[\text{Equating } A]$$

$$\frac{2}{\cos \theta} = \frac{4}{\cos \theta - 2 \sin \theta}$$

$$\frac{-\cos \theta + 2 \sin \theta}{\cos \theta} = 2$$

$$-1 + 2 \tan \theta = 2$$

$$\tan \theta = +3/2$$

$$\boxed{\theta = 56.31}$$

→ Put ϕ in (1);

$$A \cos(56.31) = 2$$

$$A = 3.61$$

So,

$$i(t) = 3.61 e^{-t} (\cos(2t - 56.31))$$

Q6: $\frac{d^2 i}{dt^2} + 3 \frac{di}{dt} + 2i = 4$

→ Source free or natural response of circuit is that response in which $V_s = 0$ and $i_s = 0$.

$$\frac{d^2 i}{dt^2} + 3 \frac{di}{dt} + 2i = 0$$

$$\frac{d^2 y(t)}{dt^2} + 2 \xi \omega_0 \frac{dy(t)}{dt} + \omega_0^2 y(t) = 0$$

→ Comparing eq (1) with eq (2);

$$2 \xi \omega_0 = 3 \quad \text{and} \quad \omega_0^2 = 2$$

$$\xi = \frac{3}{2\sqrt{2}}$$

$$\omega_0 = \sqrt{2}$$

→ $\xi = \frac{3}{2\sqrt{2}} > 1$, so an overdamped

Response. Thus,

$$\tau_1 = \frac{1}{(\xi - \sqrt{\xi^2 - 1})\omega_0} = \frac{1}{\left(\frac{3}{2\sqrt{2}} - \sqrt{\left(\frac{3}{2\sqrt{2}}\right)^2 - 1}\right)\sqrt{2}} = 1$$

$$\tau_1 = 1$$

$$\tau_2 = \frac{1}{(\xi + \sqrt{\xi^2 - 1})\omega_0} = \frac{1}{\left(\frac{3}{2\sqrt{2}} + \sqrt{\left(\frac{3}{2\sqrt{2}}\right)^2 - 1}\right)\sqrt{2}} = \frac{1}{2}$$

$$\tau_2 = 1/2$$

→ $i(t)$ and its derivative at $t=0^+$;

- $i(0^+) = 1 \text{ A}$
- $\frac{di(0)}{dt} = -1 \text{ A/s}$

→ Let us now find, on the basis of initial condition, A_1 and A_2 ;

- $i(0^+) = A_1 + A_2$

$$\boxed{1 = A_1 + A_2} \quad (1)$$

- $\frac{d(i(0^+))}{dt} = -\frac{1}{T_1} A_1 - \frac{1}{T_2} A_2$

$$-1 = -(1)A_1 - 2A_2$$

$$\boxed{A_1 = 1 - 2A_2} \quad (2)$$

→ substitute eq (1) and (2);

- $1 = 1 - 2A_2 + A_2$

$$2A_2 - A_2 = 0$$

$$\boxed{A_2 = 0}$$

- $\boxed{A_1 = 1}$

→ $i(t) = A_1 e^{-t/\tau_1} + A_2 e^{-t/\tau_2} + i_{ss}$

As $i_{ss} = i(\infty)$

and From

$$\frac{d^2 i}{dt^2} + 3 \frac{di}{dt} + 2i = 4$$

W0 $i(\infty) = 4$

$$\sqrt{2} i(\infty) = 4$$

$$\boxed{i(\infty) = 2\sqrt{2}}$$

→ Therefore,

$$\boxed{i(t) = e^{-t} + 2\sqrt{2}}$$