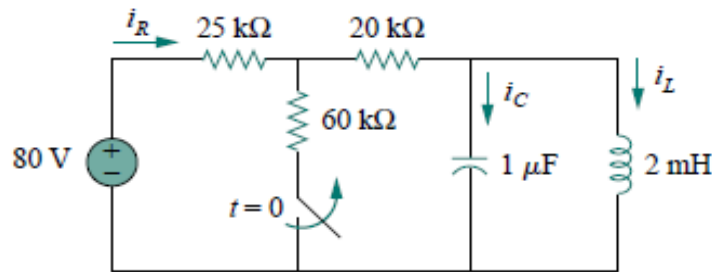


Q 1 In the circuit shown, determine $i_L(0^+)$, $i_c(0^+)$, $\frac{di_L(0^+)}{dt}$, $\frac{di_c(0^+)}{dt}$, $i_L(\infty)$, $i_c(\infty)$, also for $t > 0$ find damping ratio and comment on the kind of damping the circuit will experience.



Q 2 If the voltage across and current through a series combination of resistance and an unknown energy storage element are

$$v(t) = 15 \cos(10^6 t + 66.87^\circ) \text{ V} \quad \text{and} \quad i(t) = 3 \cos(10^6 t + 30^\circ) \text{ mA}$$

Find the resistance and unknown element. Also comment on the type of filter implemented through this circuit and find the cutoff frequency as well.

Q 3 A series RLC circuit has $R = 100\Omega$, $L = 50\mu\text{H}$ and $C = 2\text{nF}$. Find ω_0 , Q , BW, ω_L , ω_H . Find ω_1 and ω_2 at which I_m reduces to 25% of its max.

Q 4 A parallel RLC circuit has $R = 1\text{k}\Omega$, $L = 250\mu\text{H}$ and $C = 4\text{nF}$. Find ω_0 , Q , BW, ω_L , ω_H . Find ω_1 and ω_2 at which V_m reduces to 25% of its max.

Q 5 A band pass series RLC circuit is required with $f_0 = 1\text{MHz}$ and $\text{BW} = 10\text{kHz}$, given $L = 40\text{mH}$ find appropriate values of R and C .

Q 6 A series RC circuit is driven by a 100kHz 24V peak ac source. Find the appropriate values of R and C that result in $I_m = 9.39 \text{ mA}$ and $\phi = 38.5^\circ$